



Grade Sheet for Lab #1

Fall 2015.

Group Number: 10

Group Member Name: Rebecca Nite

Student Number: 260 379 389

Group Member Name: Benjamin Landry

Student Number: 260583598

Marks

2	1. Schematic diagram for the 6-bit comparator	AK
2	2. VHDL file for the 6-bit comparator	AK
2	3. Initial partial simulation results for the 6-bit comparator	AK
2	4. Complete simulation results for the 6-bit comparator	AK
2	5. Boolean equations for the 1's counter circuit	Arash
2	6. VHDL description for the 1's counter circuit	Arash
2	7. Simulation Testbench VHDL for the 1's counter circuit	AK
2	8. Simulation results for the 1's counter circuit	AK
		TA Signatures

Each part should be demonstrated to one of the TAs who will then give a grade and sign the grade sheet. Grades for each part will be either 0, 1, or 2. A mark of 2 will be given if everything is done correctly. A grade of 1 will be given if there are significant problems, but an attempt was made. A grade of 0 will be given for parts that were not done at all, or for which there is no TA signature.